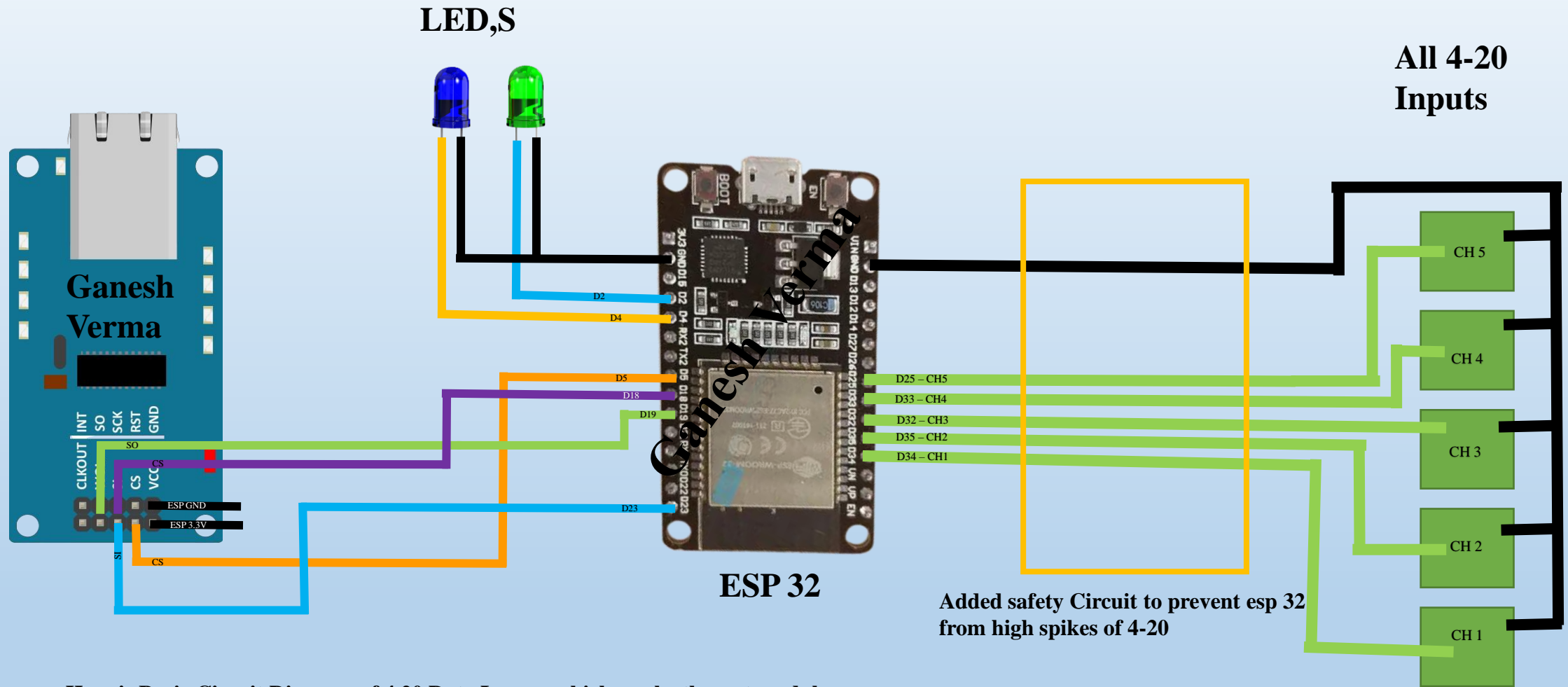


## Ethernet Module enc28j60



Here is Basic Circuit Diagram of 4 20 Data Logger which work ethernet module.  
Note: Add Safety Circuit on every input with combination of Zener diode or any SMD components Like TVS Diode According To your Need and calculations.